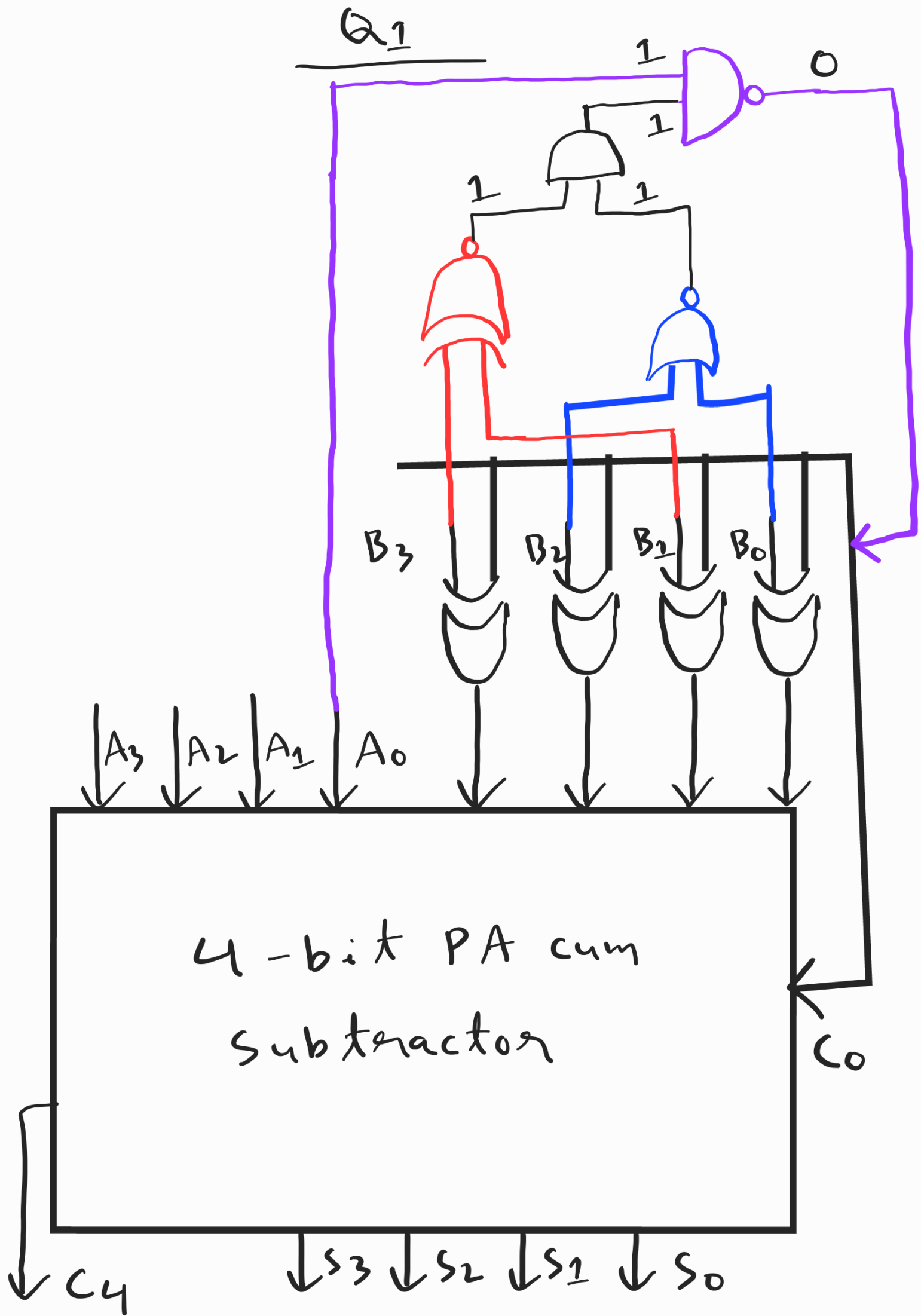




Patterns:


<u>Dec</u>	<u>B₃</u>	<u>B₂</u>	<u>B₁</u>	<u>B₀</u> (binary)
0	<u>0</u>	0	<u>0</u>	0
10	<u>1</u>	0	<u>1</u>	0

If A is odd then $A_0 \rightarrow 1$


We have to send $C_{in} = 0$

if both condition fulfills

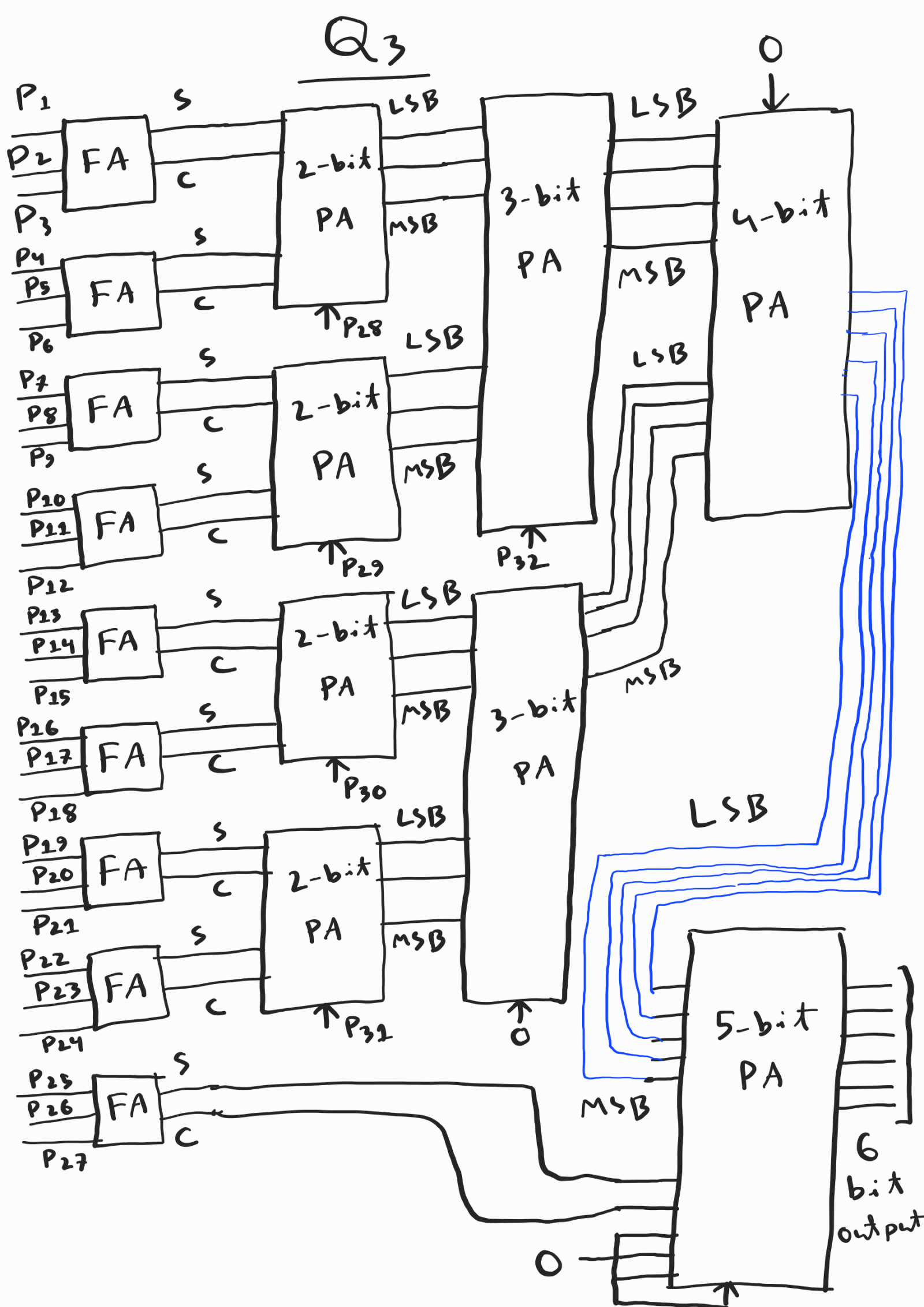
values are traced in the circuit for both conditions are true



Q4

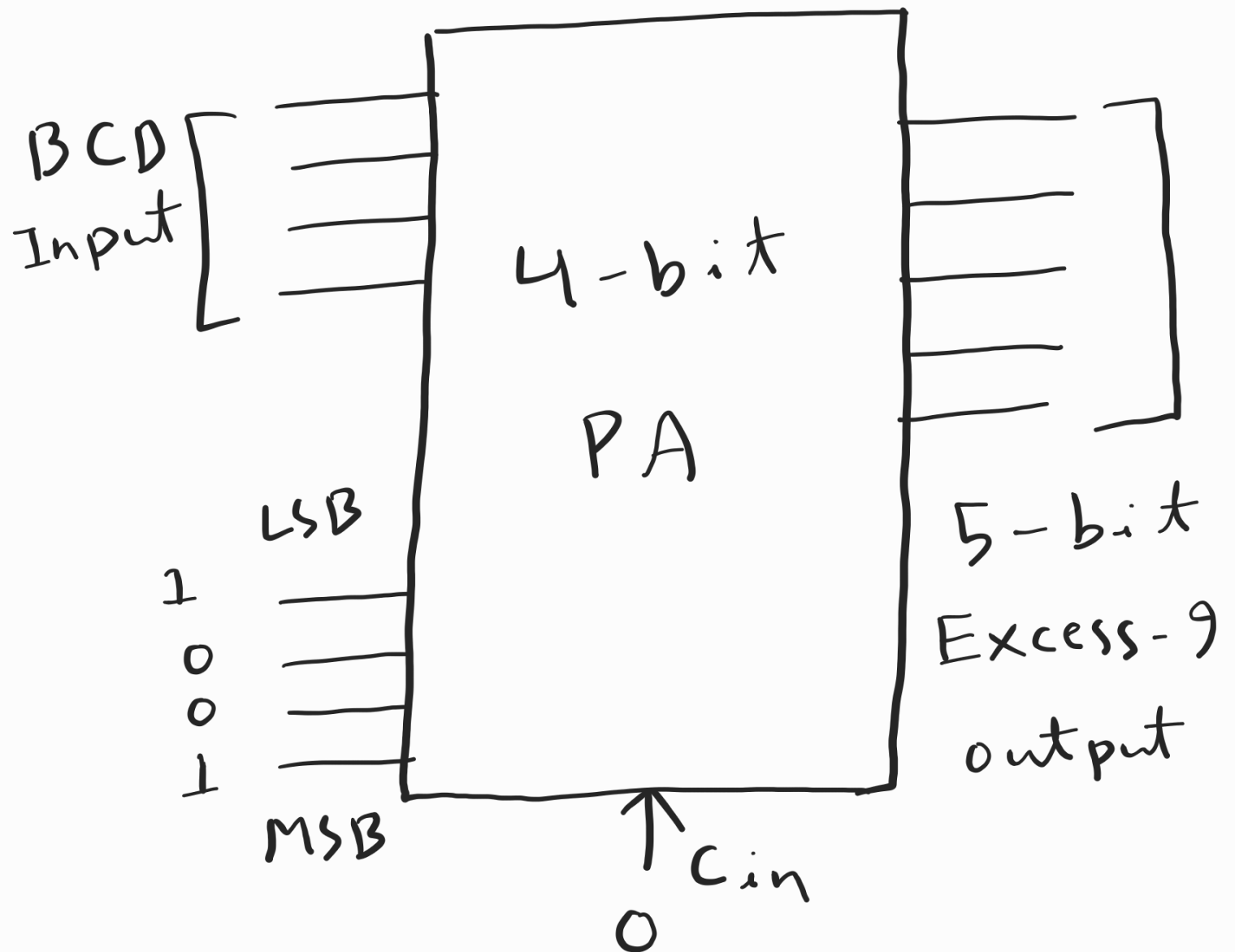


Q5

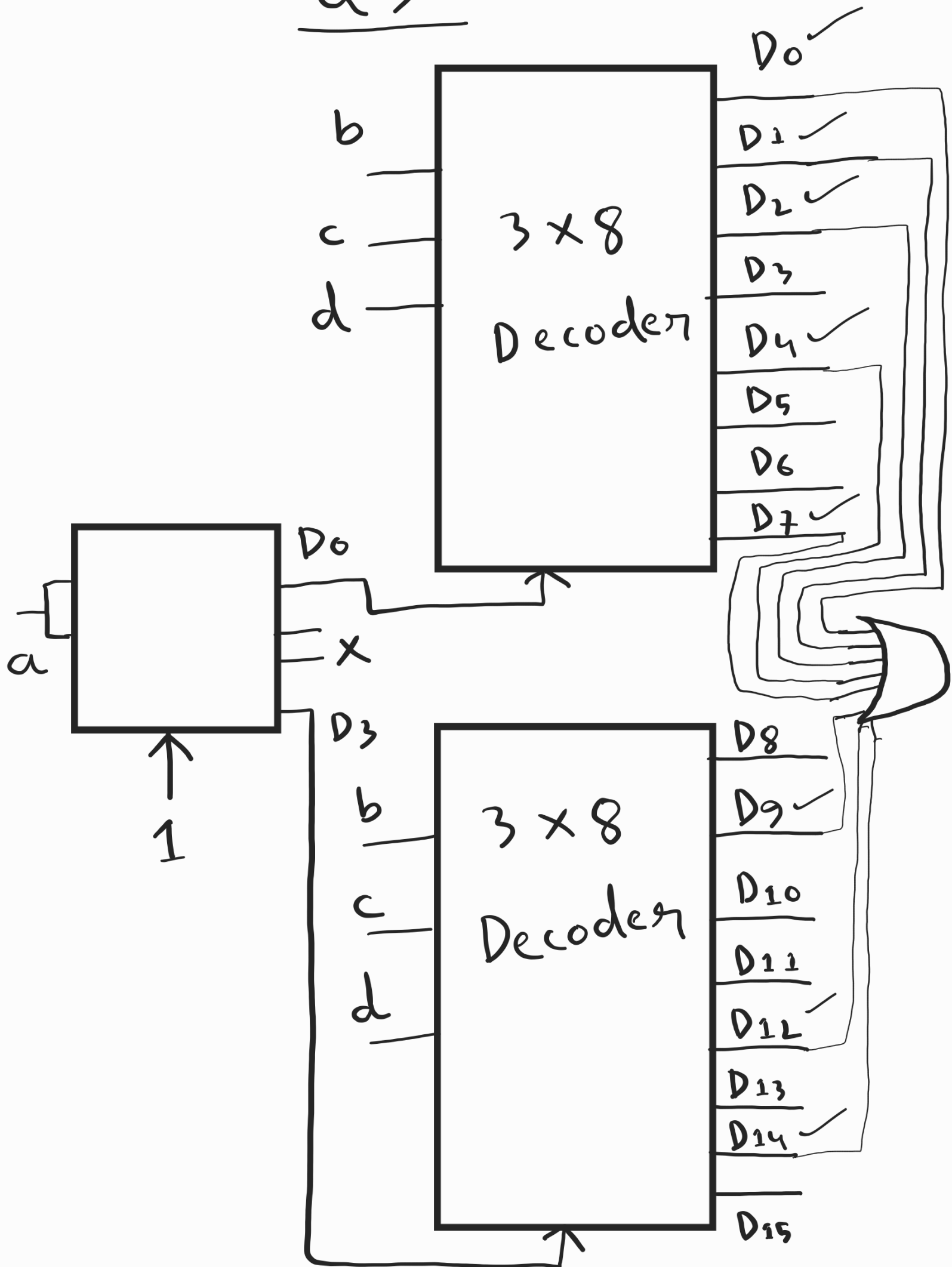


+5V

Q6 (a)

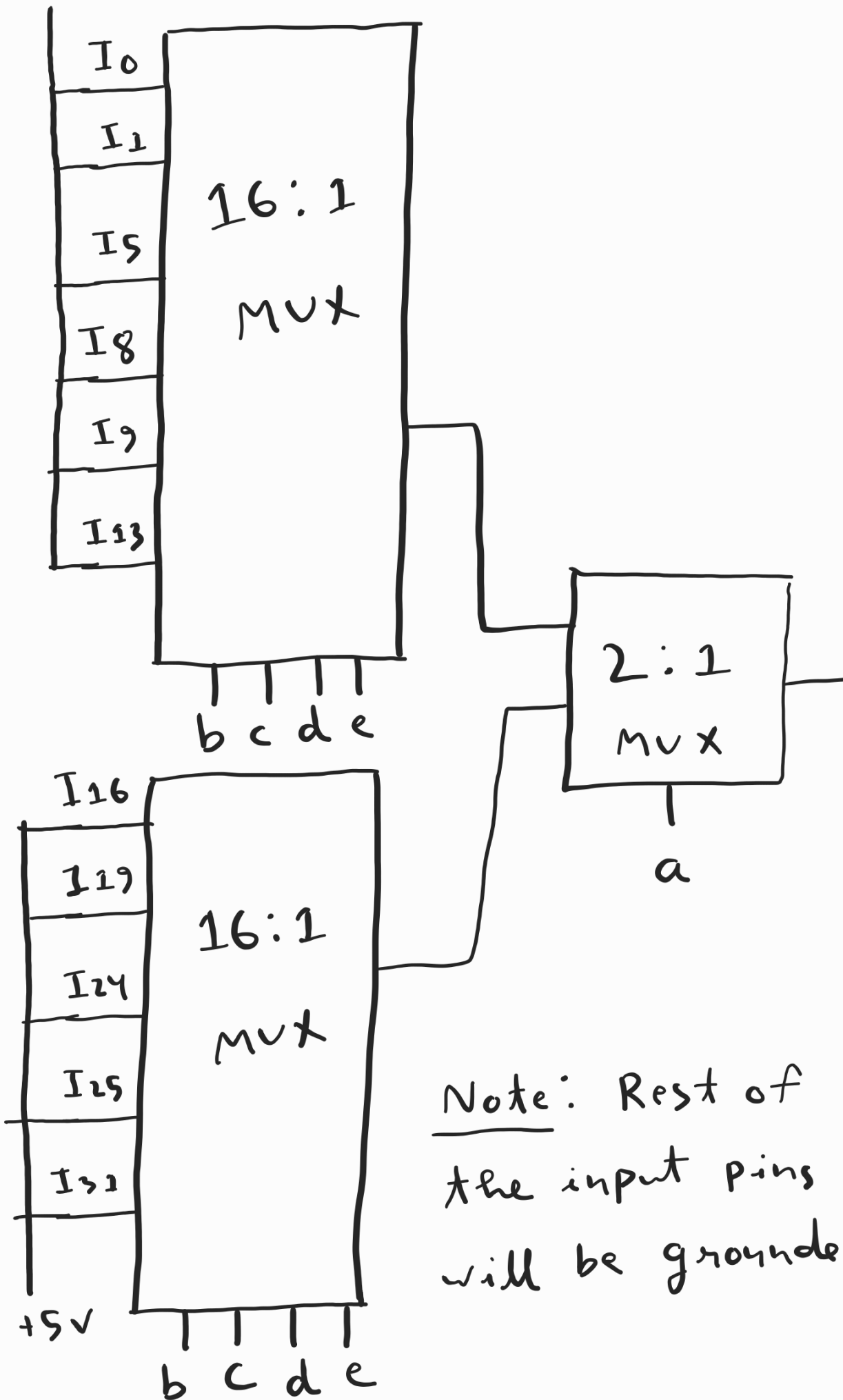


Note: Rest of the input pins will be grounded

Q6 (b)

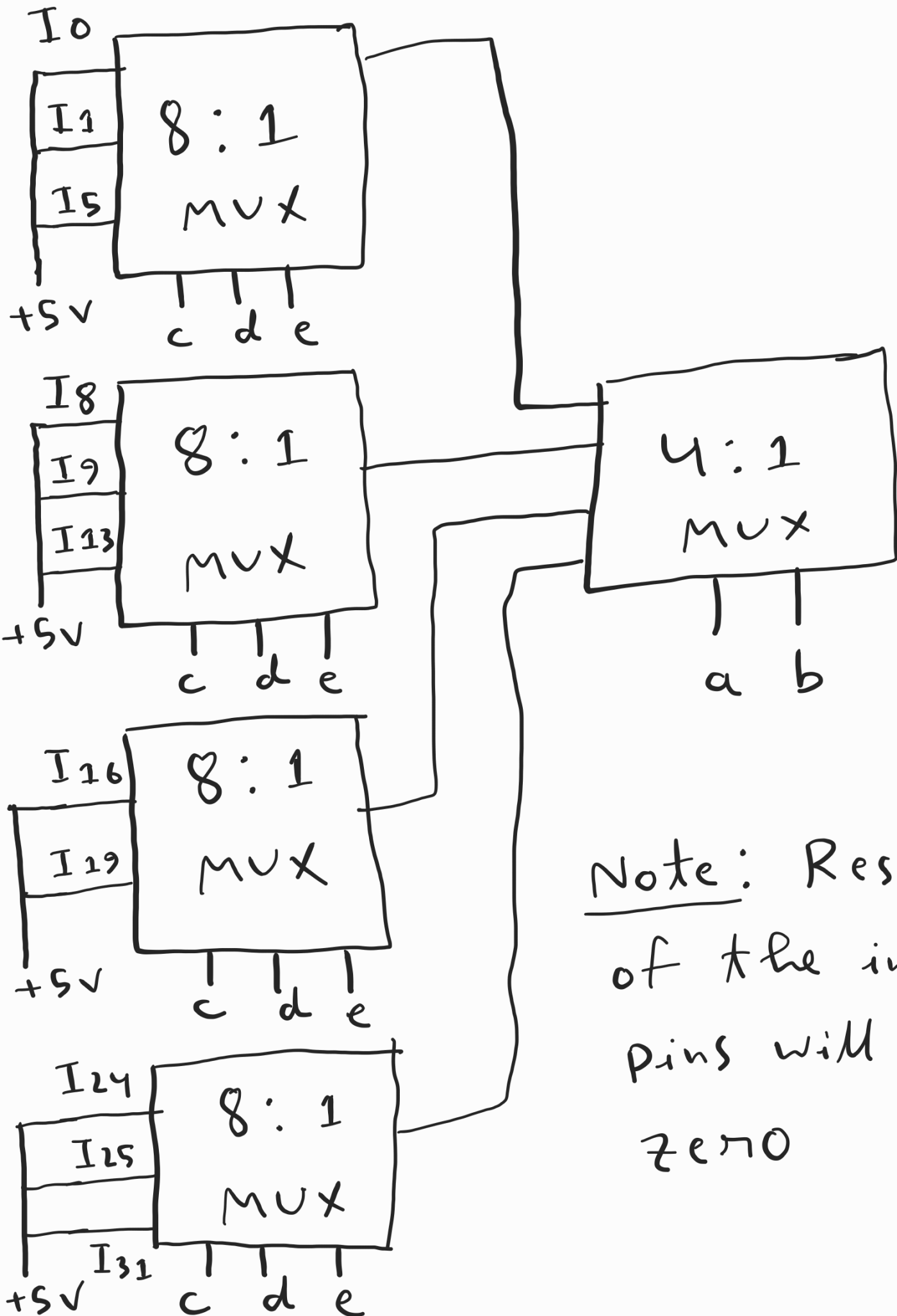

Note: Rest of the input pins will be zero

Q 7 (b)

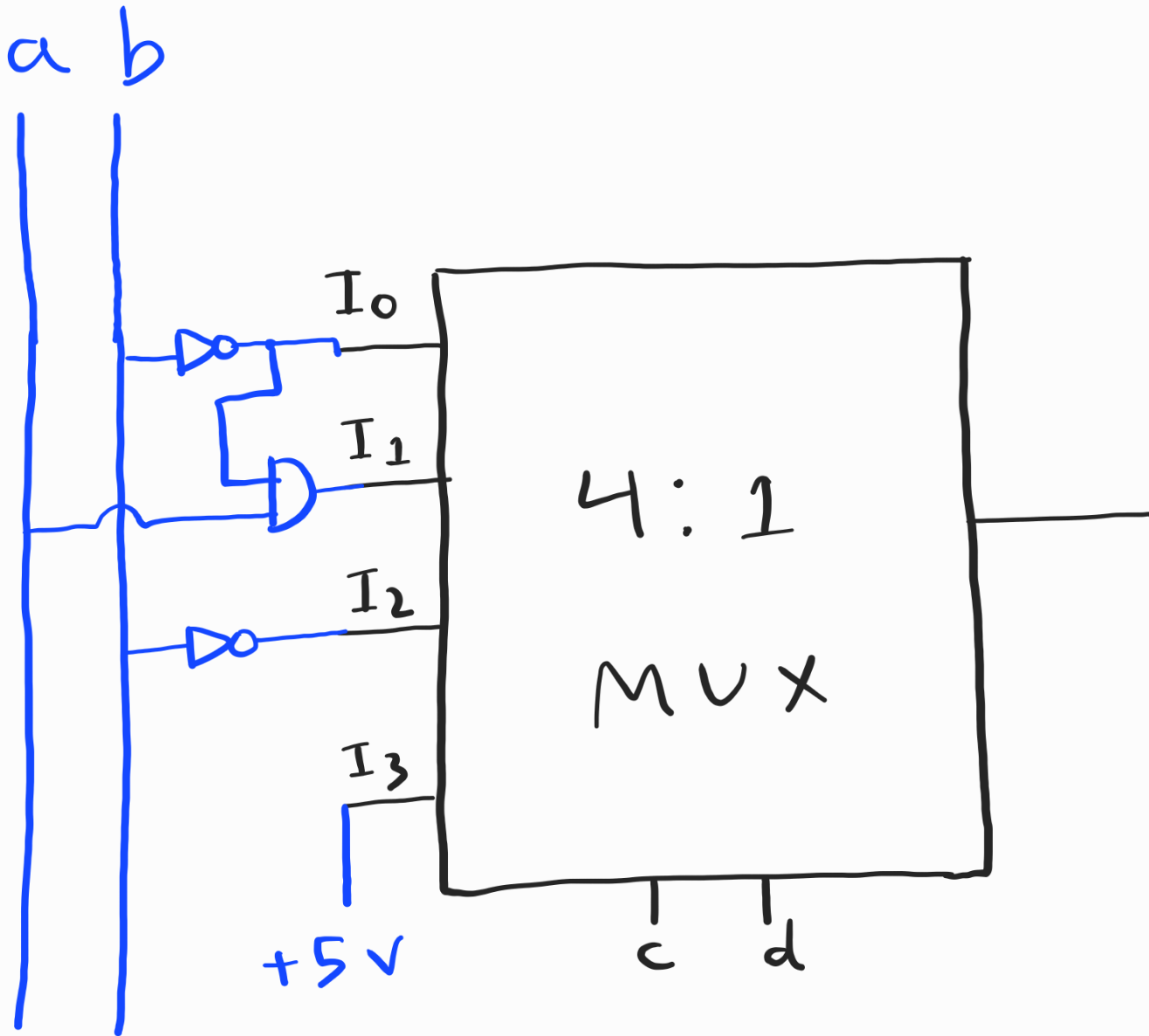

	I_0	I_1	I_2	I_3
$a'b'$	0	1	2	3
$a'b$	4	5	6	7
ab'	8	9	10	11
ab	12	13	14	15
	b'	ab'	b'	1

Q8

Solved in theory class!