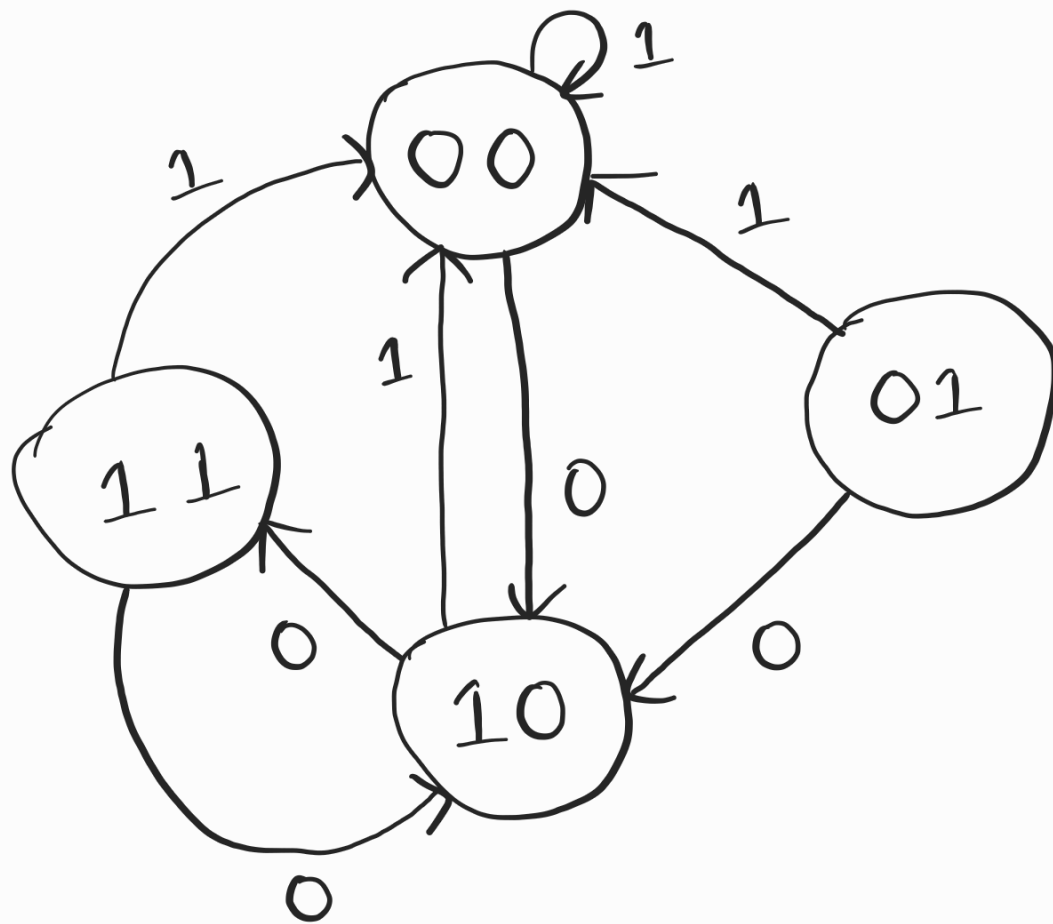


Q 1

$$J_A = A'x' \quad K_A = A' + x$$

$$D_B = (A' + x + B)'$$
$$= AB'x'$$

A	B	x	J_A	K_A	D_B	A^+	B^+
0	0	0	1	<u>1</u>	0	1	0
0	0	1	0	<u>1</u>	0	0	0
0	1	0	1	<u>1</u>	0	1	0
0	1	<u>1</u>	0	<u>1</u>	0	0	0
<u>1</u>	0	0	0	0	<u>1</u>	1	1
<u>1</u>	0	1	0	1	0	0	0
1	1	0	0	0	0	1	0
<u>1</u>	<u>1</u>	1	0	1	0	0	0




Q2

Leon $\rightarrow 00$, Claire $\rightarrow 01$, Ada $\rightarrow 10$,
Chris $\rightarrow 11$

No of states $\rightarrow 4$

No of FF required $\rightarrow \lceil \log_2^4 \rceil$
 $= 2$

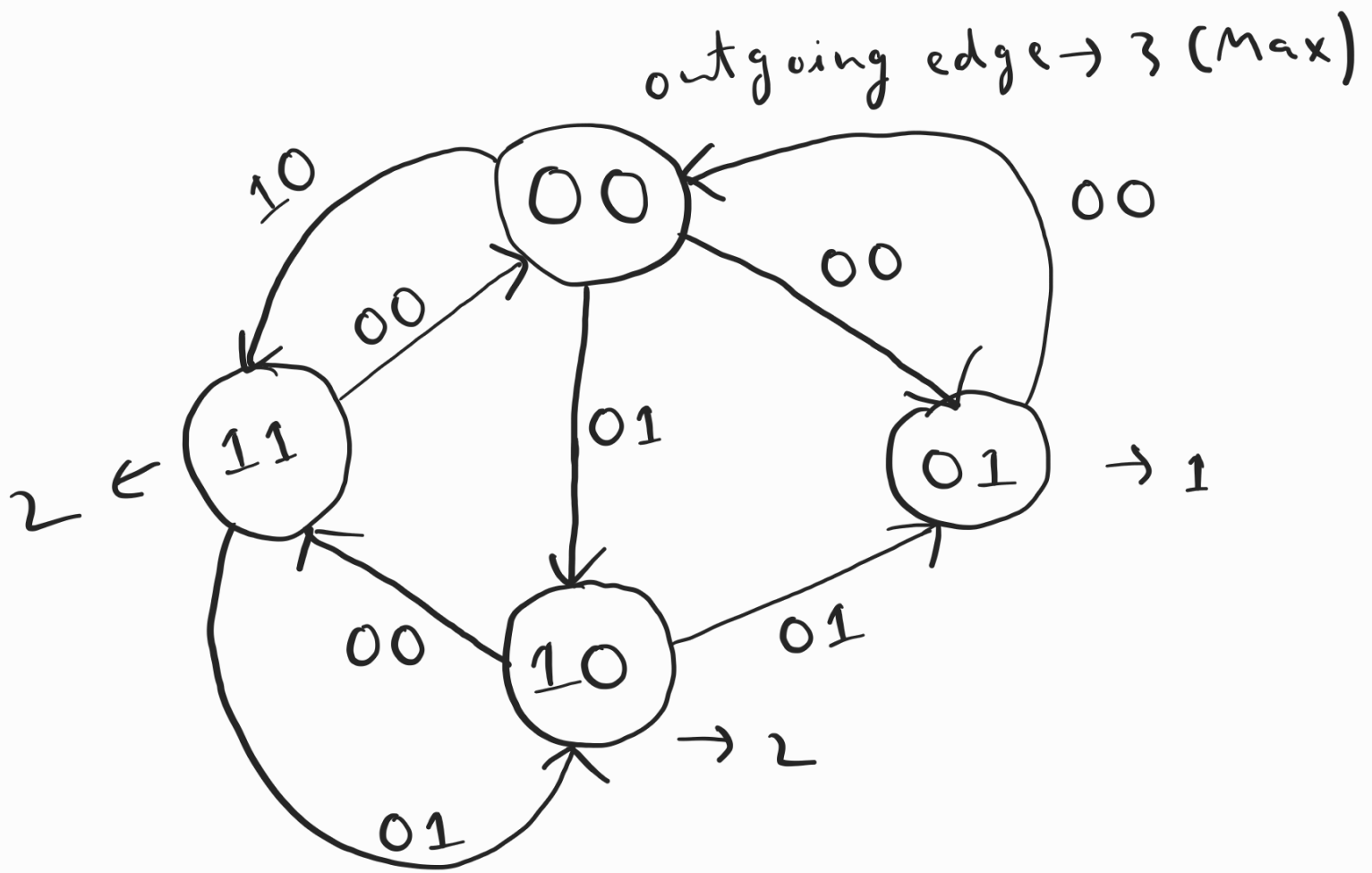No of external inputs $\rightarrow \lceil \log_2^3 \rceil$
 $= 2$
(x and y)



Present states $\rightarrow A$ and B

Next states $\rightarrow A+$ and $B+$


A	B	x	y	A^+	B^+	T_A	T_B
0	0	0	0	0	1	0	1
0	0	0	1	1	0	1	0
0	0	1	0	1	1	1	1
0	0	1	1	x	x	x	x
0	1	0	0	0	0	0	1
0	1	0	1	x	x	x	x
0	1	1	0	x	x	x	x
0	1	1	1	x	x	x	x
1	0	0	0	1	1	0	1
1	0	0	1	0	1	1	1
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	0	0	1	1
1	1	0	1	1	0	0	1
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

$$T_A = x + B'y + AB y'$$

AB \	xy	$x'y'$	$x'y$	xy'
$A'B'$	0 1	1 X	3 1	2
$A'B$	4 X	5 X	7 X	6
AB	12 1	13 X	15 X	14
AB'	8 1	9 X	11 X	10

$$T_B = y' + A$$

AB \	xy	$x'y'$	$x'y$	xy'
$A'B'$	0 1	1 X	3 1	2
$A'B$	4 1	5 X	7 X	6 X
AB	12 1	13 1	15 X	14 X
AB'	8 1	9 1	11 X	10 X

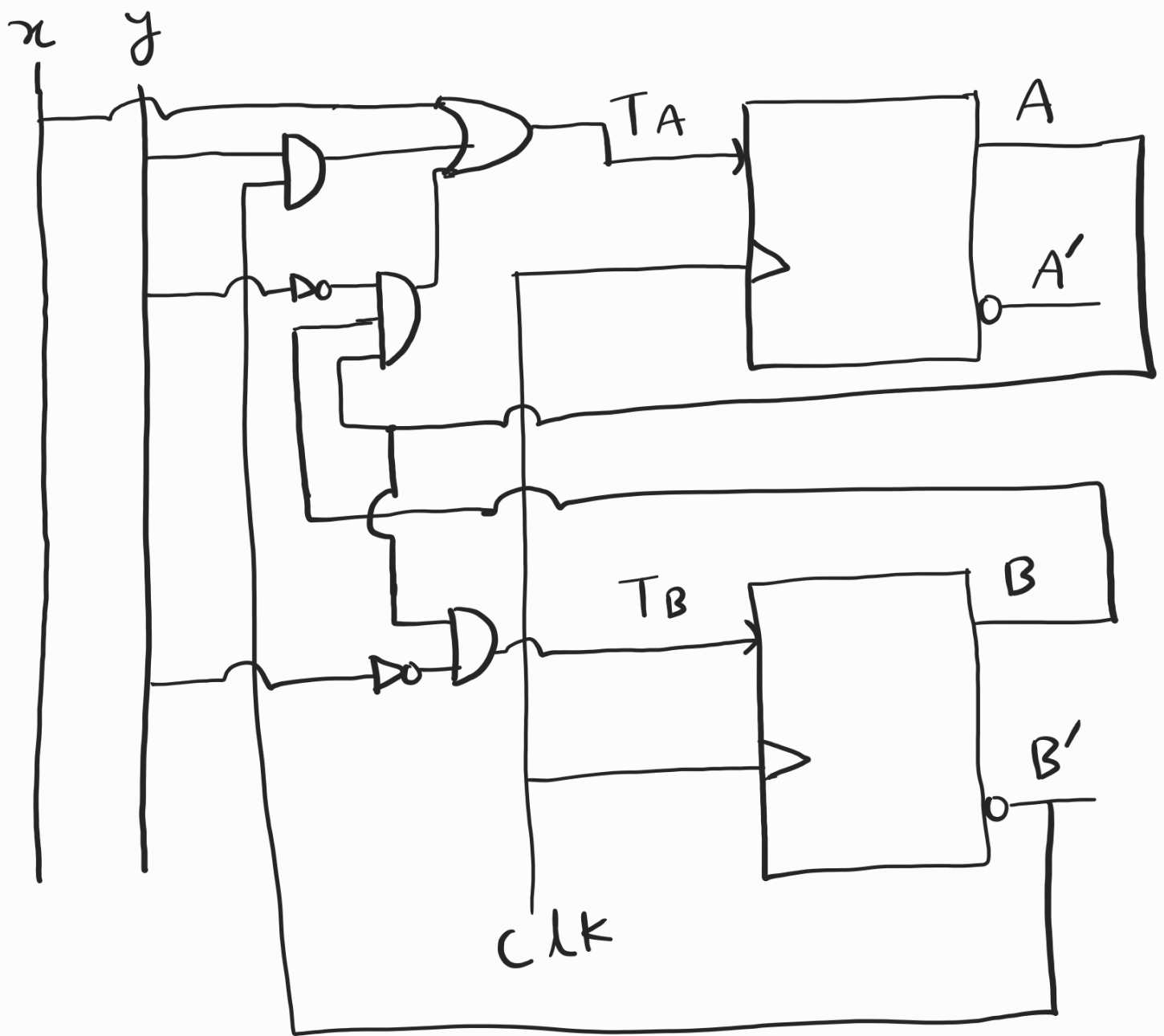

Q3

$A \rightarrow -ve$ edge

$B \rightarrow -ve$ edge

$C \rightarrow +ve$ edge

